

# Resistor Combinations

*Solving Problems by Thought rather than by Algebra*

Once you know the formulas for resistors in series and parallel, it's terribly easy to

- think that they are the only way of solving Resistor problems, and
- to make mistakes and not realise you've done so.

There are certain combinations of resistors which you should be able to just look at and say 'ah, they're obviously going to have a total resistance of ...'. Completing the tables below should help you on the way to being able to do so.

Resistors used	Connected in ...	Draw the circuit:	Total Resistance
$R$ and $R$	Series		
$R$ and $R$	Parallel		
$R$ , $R$ and $R$	Series		
$R$ , $R$ and $R$	Parallel		
$R$ , $R$ , $R$ and $R$	Series		
$R$ , $R$ , $R$ and $R$	Parallel		

Combination	$R_{\text{tot}} = ?$
$1\Omega$ in parallel with $1000\Omega$	
$10\Omega$ in parallel with $1000\Omega$	
$100\Omega$ in parallel with $1000\Omega$	
$1\Omega$ in parallel with $1\text{M}\Omega$	
$10\Omega$ in parallel with $1\text{M}\Omega$	
$100\Omega$ in parallel with $1\text{M}\Omega$	

Now summarise what you've found as a general pattern for resistors  $R_1$  and  $R_2$  in parallel where  $R_1 \gg R_2$ :

# How to become a Resistor Jedi

Building on the skills you've developed over the page, you can now work out roughly what the total resistance of any number of resistors in parallel will be, before you do a calculation to check, if necessary. This can often save time or help you spot silly mistakes by doing rough estimates before you use the formula.

## For example:

- If you have two  $10\Omega$  resistors in parallel, you know that the total resistance will be  $5\Omega$ . If you have four  $10\Omega$  resistors in parallel, you know that the total resistance will be  $2.5\Omega$ , and so on.
- If you have a  $10\Omega$  and a  $100\Omega$  resistor in parallel, you know that total resistance will be a bit less than  $10\Omega$ , because adding the  $100\Omega$  resistor just gives the current a slightly easier setup than the  $10\Omega$  by itself.  $R_{tot}$  is actually about  $9.1\Omega$
- If you have a  $10\Omega$  and a  $1000\Omega$  resistor in parallel, you know that total resistance will still be a bit less than  $10\Omega$ , but it will be closer to  $10\Omega$  than in the previous example because the resistors are more unequal, so it becomes more similar to just a  $10\Omega$  Resistor on its own.  $R_{tot}$  is actually about  $9.9\Omega$
- If you've got more than two resistors in parallel, the total resistance will just be a bit less than the resistance of the smallest resistor. The more different the resistances are, the closer  $R_{tot}$  will be to the resistance of the smallest resistor.

Now try these (*don't use the formula until you've made a sensible guess!*):

Combination	$R_{tot} = ?$ (rough guess and explanation)	$R_{tot} = ?$ (use the formula)
$50\Omega$ in parallel with $1000\Omega$		
$50\Omega$ in parallel with $10k\Omega$		
$50k\Omega$ in parallel with $10\Omega$		
$50k\Omega$ in parallel with $200\Omega$		
$50k\Omega$ in parallel with $10k\Omega$ and $200\Omega$		
$50\Omega$ , $1000\Omega$ and $10k\Omega$ , all in parallel		

Now you've honed this skill, amaze and astound your chums by looking over their shoulder whilst they're plugging away using the formula for their homework and tell them roughly what the answer will be long before they can calculate it. Or challenge people to estimate  $R_{tot}$  for a given combination and see who gets closest. Fun for all the family.